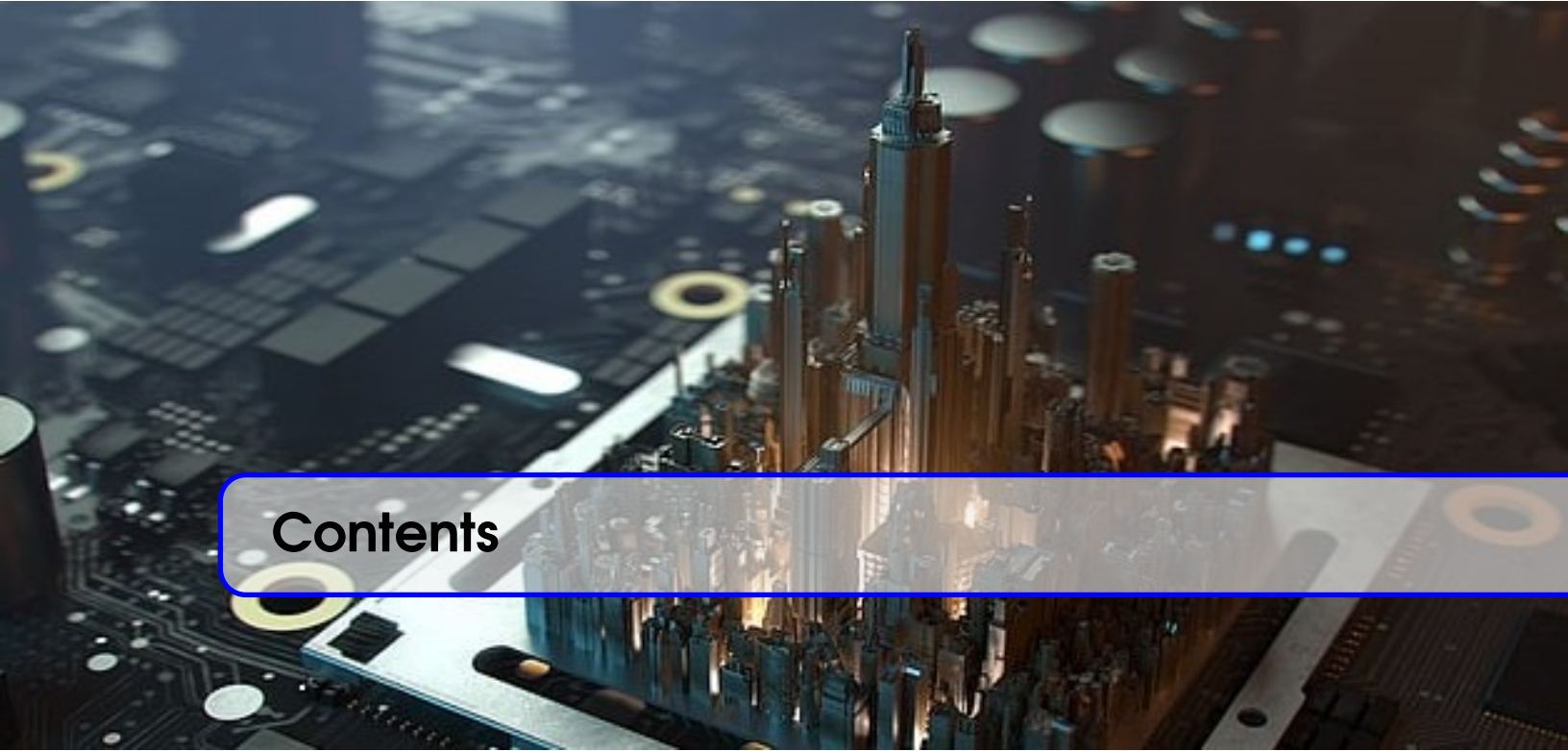




Contents

I

Part One

1	Introduction	15
1.1	Electronics	15
1.2	The Atom	15
1.3	Bohr's Atomic Model	16
1.4	Periodic Table	17
1.5	Energy Levels and Bands	17
1.6	Insulators	18
1.7	Semiconductors	19
1.8	Conductors	20
2	Semiconductors	29
2.1	Modeling Concept in Electronics	29
2.2	Covalent Bonding in Semiconductors	30
2.3	Compound Semiconductor Materials	30
2.4	Uniform Semiconductors in Equilibrium	32
2.4.1	Intrinsic semiconductors	32
2.4.2	Extrinsic semiconductors	33
2.5	Effect of Temperature on Semiconductor	38
2.6	Uniform Excitation of Semiconductors	39
2.6.1	Uniform electric field	40
2.6.2	Uniform optical excitation	46
2.7	Non-uniform Conditions	47
2.7.1	Diffusion	48

2.7.2	Excitation of non-uniformly doped semiconductor	49
3	pn Junction Diodes and Applications	53
3.1	Introduction	53
3.2	pn Junction at Equilibrium	53
3.3	Biased pn Junction	56
3.4	Terminal Characteristics of pn Junction Diodes	62
3.4.1	The forward-biased region	62
3.4.2	The reverse-biased region	62
3.4.3	The reverse break-down region	63
3.5	Diode Equivalent Circuits	63
3.5.1	The ideal diode model	64
3.5.2	Constant voltage drop diode model	64
3.5.3	Piece-Wise Linear diode model	65
3.5.4	Exponential model	66
3.5.5	Zener diode model	66
3.5.6	Small-signal diode model	68
3.5.7	High frequency model	68
3.6	Diode Applications	81
3.6.1	Rectification	81
3.6.2	Clipping circuit	86
3.6.3	Clamping circuit	89
3.6.4	Logic gates	93
3.6.5	Voltage multiplier	94
3.7	Other Diodes	96
3.7.1	Light Emitting Diode (LED)	96
3.7.2	Photodiodes	97
3.7.3	Varactors	97
3.7.4	Schottky-Barrier diode (SBD)	97
4	Introduction to MATLAB and LTspice	103
4.1	Introduction	103
4.2	LTspice	103
4.2.1	Installation	104
4.2.2	LTspice: Using the net-list environment	104
4.2.3	Writing the net list command	105
4.2.4	LTspice: Using the schematic editor	106
4.3	MATLAB	106
4.3.1	MATLAB: Syntax and descriptions	108
4.3.2	MATLAB operations	108
4.3.3	Writing m-files	109
4.3.4	Syntax for writing function file and some MATLAB commands	109

4.4	pn Diode Characterisation 1	110
4.5	pn Diode Characterization 2	111
4.6	Effects of Temperature	114
4.7	Effect of Intrinsic Concentration	115
4.8	Voltage-multiplier Operation	116
4.9	Power Supply	117

II

Part Two

5	Bipolar Junction Transistors (BJTs)	121
5.1	Introduction	121
5.2	Construction	121
5.3	Operation	123
5.4	Ebers-Moll Model of BJTs	126
5.5	BJT Configuration and Device Characteristics	128
5.5.1	Common-base configuration	128
5.5.2	Common-emitter configuration	129
5.5.3	Common-collector configuration	131
5.6	BJT's Operating Point	133
5.7	BJT Circuit Biasing for Signal Amplification	137
5.7.1	The fixed-bias circuit	138
5.7.2	The emitter-stabilized bias circuit	141
5.7.3	Voltage-divider bias circuit	145
5.7.4	Collector-feedback bias circuit	151
5.8	Q-Point or DC Stabilization Factor	154
5.8.1	Stability factor for fixed-bias configuration	156
5.8.2	Stability factor for emitter-bias configuration	157
5.8.3	Stability factor for voltage-divider bias configuration	158
5.9	Q-Point Variation with Circuit Parameters	160
5.10	Typical Design Examples of BJT Amplifiers	162
5.11	Additional worked examples on BJTs	165
5.12	BJT Biasing for Switching Circuits	170
6	Field Effect Transistors (FET)	179
6.1	Introduction	179
6.2	JFET	180
6.2.1	Construction	180
6.2.2	Operation	180
6.2.3	Transfer characteristics of JFET	184
6.2.4	JFET operating regions	185
6.2.5	JFET circuit configurations	188
6.2.6	JFET biasing	188

6.3	MOSFET	200
6.3.1	DMOSFET	200
6.3.2	EMOSFET	206
6.4	Typical Design Examples of FET Amplifiers	218
6.5	VMOS and CMOS	220
6.5.1	VMOS	220
6.5.2	CMOS	221
7	Small-Signal Analysis for BJT and FET circuits	229
7.1	Introduction	229
7.2	Important Metrics in AC Analysis	229
7.2.1	Input impedance	230
7.2.2	Output impedance	232
7.2.3	Voltage gain	233
7.2.4	Current gain	234
7.2.5	Phase shift	234
7.3	Two-Port Networks	237
7.4	Hybrid Equivalent Model	238
7.4.1	Common-base hybrid model	240
7.4.2	Common-emitter hybrid model	240
7.5	r_e parameter transistor model	241
7.5.1	Common-base r_e model	242
7.5.2	Common-emitter r_e model	244
7.5.3	Common-collector configuration	246
7.5.4	Similarity of the hybrid and r_e model	247
7.6	BJT: AC analysis (Worked Examples)	250
7.7	Loaded BJT Amplifier with Applied Signal Source	268
7.7.1	Fixed-bias configuration	268
7.7.2	Voltage-divider bias configuration	271
7.7.3	Voltage-divider configuration with emitter unbypassed	272
7.7.4	Emitter-follower configuration	274
7.8	FET: AC Signal Modelling	277
7.8.1	JFET AC signal modelling	278
7.8.2	FET AC equivalent circuit for common-source	279
7.8.3	FET AC equivalent circuit for common-drain	284
7.8.4	FET AC equivalent circuit for common-gate	286
7.9	DMOSFET AC Signal Modeling	288
7.10	EMOSFET AC Signal Modeling	289
8	Special Amplifiers	299
8.1	Introduction	299
8.2	Classification of Amplifiers	299
8.2.1	Based on the number of stages	299
8.2.2	Based on the magnitude of the input signal	300

8.2.3	Based on its usage or output	300
8.2.4	Based on the frequency range	300
8.2.5	Based on the coupling method	301
8.2.6	Based on the transistor configuration	301
8.2.7	Based on the conduction angle	301
8.3	Multistage Amplifier	302
8.3.1	Cascade connection	302
8.3.2	Cascode connection	308
8.3.3	Darlington pair connection	310
8.4	Differential Amplifiers	316
8.4.1	Operation of differential amplifier	317
8.4.2	Single-ended input signal operation	317
8.4.3	Double-ended differential mode input signal operation	320
8.4.4	Double-ended common-mode input signal operation	322
8.4.5	DC analysis of differential amplifier	323
8.4.6	AC analysis of differential amplifier	325
8.4.7	AC analysis of common-mode amplifier	327
8.5	Power Amplifiers	329
8.5.1	Power efficiency	330
8.5.2	Total Harmonic Distortion (THD)	330
8.5.3	Heat dissipation	330
8.5.4	Power amplifier categories	331
9	Amplifier Frequency Response	345
9.1	Introduction	345
9.2	Frequency Response Fundamentals	345
9.2.1	The decibel	345
9.2.2	Signal representation in dBW, dBm and dBV	347
9.2.3	Cutoff frequency and Bandwidth	350
9.2.4	Octave and Decade	350
9.3	Review of First-Order Filters	351
9.3.1	Low-pass (LP) filters or lag network	351
9.3.2	High-pass (HP) filters or lead network	353
9.3.3	Frequency response of low-pass filter (lag network)	355
9.3.4	Frequency response of high-pass filter (lead network)	356
9.3.5	Bode plot overview	357
9.4	Frequency Response for Combined Network Elements	358
9.4.1	Combined elements with different critical frequencies	358
9.4.2	Combined elements with the same critical frequencies	359
9.5	Frequency Response of BJT and FET Amplifiers	360
9.5.1	Frequency response of BJT amplifier	361
9.5.2	Frequency response of FET amplifiers	371
9.6	Square wave testing of Amplifier	381

10	Simulation Part II	385
10.1	Introduction	385
10.2	Plotting BJT Characteristic Curves using EM's Model	385
10.3	Determining the Q-point of FET	385
10.4	Plotting BJT Characteristic Curves with LTSpice	386
10.5	DC Operating Point	388
10.6	BJT Single-Stage Amplifier	389
10.7	BJT Two-Stage Amplifier Design	391
10.8	FET Amplifier Design	393

III

Part Three

11	Operational Amplifier	399
11.1	Introduction	399
11.2	Modeling an Op-Amp	400
11.3	Op-Amp Input Modes	402
11.4	Need for Feedback in Op-Amps	404
11.5	Effect of Negative Feedback	407
11.6	Ideal Op-Amp Characteristics	408
11.7	Op-Amp Configurations and Applications	409
11.7.1	Non-inverting Op-Amp	409
11.7.2	Inverting Op-Amp	411
11.7.3	Buffer Op-Amp	414
11.7.4	Summing amplifier	414
11.7.5	Digital-to-Analogue Converter	415
11.7.6	Difference amplifier (Subtractor)	418
11.7.7	Integrator	419
11.7.8	Differentiator	420
11.7.9	Instrumentation amplifier	421
11.7.10	Logarithm amplifier	422
11.7.11	Antilogarithm or Exponential amplifier	423
11.7.12	Comparator	424
11.7.13	Schmitt trigger	426
11.7.14	Active filters	427
11.8	Op-Amp Parameters	428
11.8.1	DC Offset Voltage	430
11.8.2	Input Offset Voltage Drift	430
11.8.3	Input Bias Current	430
11.8.4	Input Offset Current	430
11.8.5	Gain-Bandwidth Product	431
11.8.6	Unity Gain-Bandwidth	431
11.8.7	Slew rate	431

12	Oscillators	435
12.1	Introduction	435
12.2	Oscillatory Circuit	435
12.2.1	LC Oscillator	436
12.2.2	Crystal oscillator	437
12.3	Theory of Oscillation	439
12.4	Classification of Oscillators	440
12.5	Sinusoidal Oscillators	441
12.5.1	Wien bridge oscillator	441
12.5.2	RC Phase-shift oscillator	443
12.5.3	Twin-T oscillator	445
12.5.4	Colpitts oscillator	447
12.5.5	Hartley oscillator	450
12.5.6	Crystal oscillator	451
12.6	Relaxation Oscillators	452
12.6.1	Triangular wave oscillator	452
12.6.2	Voltage-Controlled oscillator (VCO)	454
12.7	Multivibrators	455
12.7.1	The 555 Timer	455
12.7.2	Astable Multivibrator using 555 timer	457
13	Analogue Filters	461
13.1	Introduction	461
13.2	Review of Transfer Function and Bode Plot	461
13.2.1	Transfer function	462
13.2.2	Bode plot	465
13.3	Filter Specifications	472
13.4	Circuit Resonance	477
13.4.1	Series resonance	477
13.4.2	Parallel resonance	479
13.5	Filter Classifications	482
13.5.1	Based on attenuation of the input signal	482
13.5.2	Based on input signal type	483
13.5.3	Based on components used	483
13.5.4	Based on filter response approximation	483
13.5.5	Based on the order or steepness	484
13.6	Passive Filters	484
13.6.1	Low-pass filters	485
13.6.2	High-pass filters	485
13.6.3	Band-pass filters	487
13.6.4	Band-reject filters	488

13.7	Active Filters	491
13.7.1	Low-pass filters	491
13.7.2	High-pass filters	493
13.7.3	Band-pass filters	493
13.7.4	Band-reject filters	494
13.8	Special Designs of Active Filters	499
13.8.1	Sallen-key filter	500
13.8.2	State-variable active filter	502
13.8.3	Multiple-feedback filter	503
13.9	Comparison of Active and Passive Filters	506
13.10	Scaling Concept in Filter Design	506
13.10.1	Magnitude scaling	507
13.10.2	Frequency scaling	508
14	Simulation Part III	515
14.1	Introduction	515
14.2	Basic Operation of Op-Amp Circuit	515
14.2.1	Inverting Amplifier	515
14.2.2	Voltage follower	516
14.2.3	Integrator	516
14.2.4	Adder	519
14.3	Band Stop Filter	519
14.4	Active Filters	520
14.5	Fourth-Order Low-Pass Filter	521
14.6	Low-Pass Sallen-Key Filter	521
14.7	Band-Pass Filter Design	522

IV

Trends in Electronics

15	Trends in Electronics: Exploring the Frontier of Nanoelectronics	525
15.1	Introduction	525
15.2	Foundations of Nanoelectronics	525
15.2.1	Nanotechnology and nanoscale materials	526
15.2.2	Quantum mechanics and its significance	527
15.2.3	Nanofabrication techniques	528
15.3	Current Trends in Nanoelectronics	529
15.3.1	Moore's law and beyond	529
15.3.2	Nanoscale transistors and beyond CMOS	530
15.3.3	Nanoscale sensors and actuators	530
15.3.4	Nanophotonics and optoelectronics	530
15.3.5	Quantum computing and quantum electronics	530
15.3.6	Wearable and flexible electronics	530

15.4	Challenges in Nanoelectronics	530
15.4.1	Manufacturing and scalability	530
15.4.2	Integration and interconnects	531
15.4.3	Reliability and device lifetimes	531
15.4.4	Energy efficiency and power consumption	531
15.4.5	Materials Compatibility and Stability	531
15.4.6	Safety and environmental considerations	531
15.5	Applications of Nanoelectronics	531
15.5.1	Nanomedicine and biomedical devices	531
15.5.2	Internet of Things (IoT) and smart devices	531
15.5.3	Energy harvesting and storage	532
15.5.4	Communication and networking	532
15.5.5	Quantum information processing	532
15.5.6	Nanoscale robotics and automation	532
15.6	Future Prospects and Emerging Concepts	532
15.6.1	Nanoelectronics beyond Moore's law	532
15.6.2	2D materials and their potential	532
15.6.3	Bio-inspired and neuromorphic computing	532
15.6.4	Exploring quantum phenomena for electronics	533
15.6.5	Integration of nanoelectronics with other disciplines	533
15.7	Conclusion	533
16	Nonotransistor: The Evolving Perspective	535
16.1	Introduction	535
16.2	Migration from Classical Physics to Quantum Physics	536
16.3	Transition from Drift and Diffusion Flow to Ballistic Flow	536
16.4	Energy Band Perspective of Electron Flow in FET	537
16.4.1	Independent energy band diagram	538
16.4.2	Energy band diagram under equilibrium conditions	538
16.4.3	Energy band diagram under gate bias	538
16.4.4	Energy band diagram under gate and drain bias	538
16.5	Density of State Perspective of Electron Flow in FET	539
16.6	Channel Conductance	541
16.6.1	Diffusive conductance	542
16.6.2	Ballistic conductance	542
16.6.3	Relationship between the ballistic and the diffusive conductance	543
16.7	Elastic Resistor	543
16.8	Landauer's Current Flow Model	544
	Index	547